


Logic gates

A.C. NORMAN

anorman@bishopheber.cheshire.sch.uk


Remember that a '1' means 'on' and a '0' means 'off'.

NOT gate

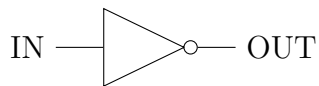


IN	OUT
0	
1	

AND gate

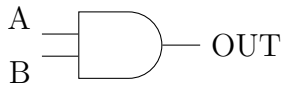

A	B	OUT
0	0	
0	1	
1	0	
1	1	

OR gate

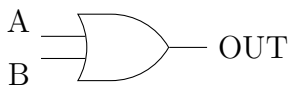

A	B	OUT
0	0	
0	1	
1	0	
1	1	



Except where otherwise noted, this work is licensed under <http://creativecommons.org/licenses/by-nc-sa/3.0/>