

# On capacitor charging

A.C. NORMAN



ACN.Norman@radley.org.uk

## Warm-up problems

1. What is the formula for how the voltage across a capacitor which is being charged varies with time? Be very careful to show what each symbol means.
2. Find out what a *supercapacitor* is. What are its advantages over a battery in an application such as electric cars?

## Regular problems

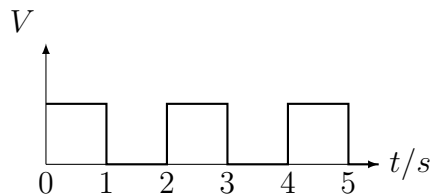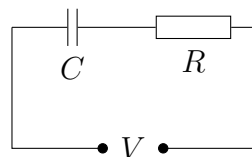3. A capacitor of capacitance  $200\text{ }\mu\text{F}$  is charged through a resistor of resistance  $300\text{ k}\Omega$ .
  - (a) What is the time constant for this circuit?
  - (b) How long will the capacitor take to charge to (i) 50%, (ii) 75%, (iii) 90% and (iv) 99.9% of a full charge?
4. (from Nelkon & Parker) The circuit below shows a capacitor  $C$  and a resistor  $R$  in series. The applied voltage varies with time as shown. The product  $CR$  is of the order 1 s. Sketch graphs showing the way the voltages across  $R$  and  $C$  vary with time. If the product  $CR$  were made considerably smaller than 1 s what would be the effect on the graphs?




5. A  $4.5\text{ V}$  battery pack is connected to a  $220\text{ }\mu\text{F}$  capacitor through a resistance of  $220\text{ k}\Omega$  by a student wishing to investigate the charging of a capacitor.
  - (a) What is the initial current?
  - (b) What is the current after one minute?
  - (c) What is the voltage after two minutes?
  - (d) How long does it take for the voltage to get to (i)  $3.0\text{ V}$  (ii)  $4.0\text{ V}$ ?
  - (e) What is the current at each of these times?
  - (f) How much energy is stored in the capacitor at each of these times?

6. Copy and complete the following table. If the graph is not going to be a straight line, write 'not straight' instead of the gradient (*Hint: you might like to try Isaac Physics A6*)

Equation	Plotted on $y$	Plotted on $x$	$y$ -intercept	Gradient
$Q = Q_0(1 - e^{-t/RC})$	$Q$	$t$		
$V = V_0 e^{-t/RC}$	$\ln(V)$	$t$		
$Q = Q_0(1 - e^{-t/RC})$	$Q$	$t$		
$I = I_0 e^{-t/RC}$	$I$	$e^{t/RC}$		

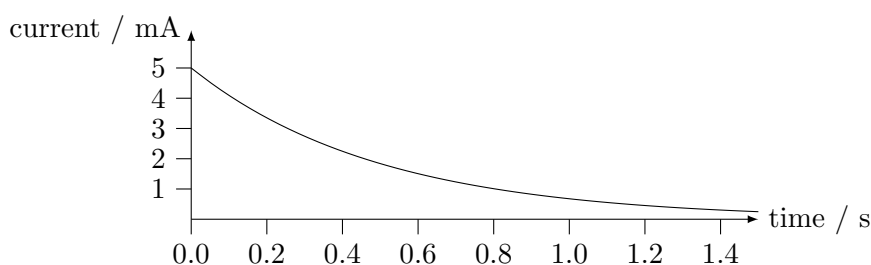
7. Show that when a battery is used to charge a capacitor through a resistor, the heat dissipated in the resistor in the circuit is equal to the energy stored in the capacitor.
8. Examine the graph below, of the current through a capacitor.



- (a) Estimate the physical quantity corresponding to the area under the graph.
- (b) What was the initial current? Was the capacitor charging or discharging?
- (c) What is the time constant? If the resistor was  $470\ \Omega$ , what was the capacitance?
- (d) What voltage is this capacitor charged up to?

## Extension problems

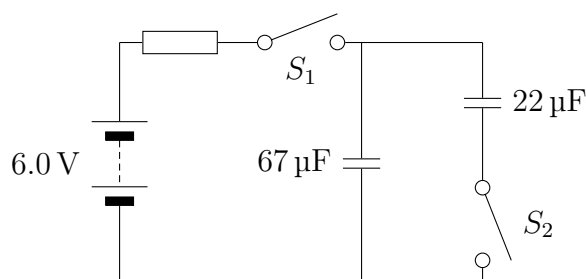9. (from CEA advanced extension award question) A feature of circuits containing charged capacitors is that there is often a spark at the contacts when a switch is opened or closed. In the circuit below the capacitors are initially uncharged and both switches are open.



Initially, switch  $S_1$  is closed, charging the  $67\ \mu\text{F}$  capacitor from the battery.  $S_1$  is then opened, leaving the  $67\ \mu\text{F}$  capacitor fully charged and the  $22\ \mu\text{F}$  capacitor still uncharged. When switch  $S_2$  is closed, a spark occurs at the contacts of this switch. Estimate the energy dissipated in this spark. Is your value likely to be an over-estimate or an under-estimate? Give a reason.



Except where otherwise noted, this work is licensed under <http://creativecommons.org/licenses/by-nc-sa/4.0/>