

Resistor networks

A.C. NORMAN

anorman@bishopheber.cheshire.sch.uk

Since a current is a flow of electrons, and the electrons cannot \leftarrow from the wire, the current in a series circuit is the same everywhere. Electrical components do not \leftarrow current, e.g. in a lightbulb, the electrons flow through the bulb and out the other side, and so the current leaving the bulb is the same as the current entering it.


At a junction of wires, some of the electrons entering the junction will flow one way, and some another way, but because the number of electrons flowing into the junction has to be the same as the number leaving it, the currents into and out of the junction will be the same.

Resistor networks

It is often necessary to find the total resistance of some complicated bunch of resistors in an electrical circuit. There are rules to help us with this, however.

Resistors in series

 For resistors in series, we simply add the resistances along the path of the current. For N resistances,



Resistors in parallel

For N resistors in parallel, the resistance is the same as the resistance of one resistor, as the number of resistors increases, as the current \leftarrow .



Except where otherwise noted, this work is licensed under <http://creativecommons.org/licenses/by-nc-sa/3.0/>