

# On internal resistance

A.C. NORMAN

ACN.Norman@radley.org.uk


## Warm-up problems

1. Explain how the formula


$$\varepsilon = IR + Ir$$

is arrived at, including what the various terms mean. It can sometimes be written as  $V = \varepsilon - Ir$ . What does the  $V$  represent, and what is the combination  $Ir$ ?

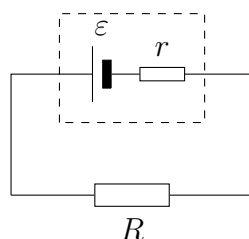2. Explain the following diagram. What does the dashed box represent, and where might you place a voltmeter to measure the *terminal p.d.*?



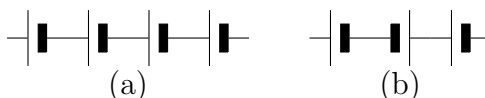
3. Each of the cells shown below has e.m.f.  $1.5\text{ V}$  and internal resistance  $0.3\Omega$ . What is the e.m.f. and internal resistance of the battery combination in each case?



## Regular problems

4. (a) Does the internal resistance of a battery increase or decrease its terminal voltage when it supplies current? Justify your answer.  
(b) What non-physical (silly) results might a too-simplistic model of a battery, which does not account for the effects of internal resistance, lead to?
5. A high resistance voltmeter reads  $3\text{ V}$  when connected across the terminals of a battery on an open circuit (no other components are connected) and  $2.6\text{ V}$  when the battery sends a current of  $0.2\text{ A}$  through a lamp. What is
  - (a) the e.m.f. of the battery,
  - (b) the terminal p.d. of the battery when supplying  $0.2\text{ A}$ ,

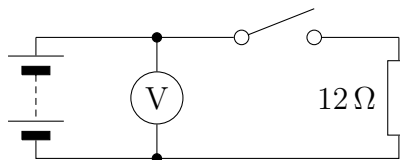- (c) the 'lost volts',  
 (d) the internal resistance of the battery,  
 (e) the resistance of the lamp?
6. In the following circuit, the voltmeter has a very high resistance. It reads 6 V when the switch is open and 4.8 V when it is closed. What is the e.m.f. and internal resistance of the battery?



7. (WJEC PH1 June 2013 Q3) A student carries out an experiment to determine the emf and internal resistance of a cell. The pd across the cell is measured when it is supplying various currents. The following readings are obtained.

current / A	0.20	0.42	0.66	0.96	1.20
p.d. / V	1.31	1.13	0.93	0.68	0.48

- (a) Plot these results on the grid (p.d. on the  $y$ -axis and current on the  $x$ -axis) and draw a line through your points.
- (b) Use your graph to determine
- the e.m.f. of the cell,
  - the internal resistance of the cell.
- (c) The cell is then connected to a torch bulb of resistance  $6.0\ \Omega$  for 20 minutes. Calculate the charge that flows through the bulb in this time. Assume the emf remains constant.
8. (WJEC PH1 June 2014 Q3) A torch battery converts 6480 J of chemical energy into electrical energy while supplying a current of 0.15 A for 2 hours. In this time only 5932 J of this energy is supplied to the bulb. Calculate
- the charge that flows,
  - the e.m.f. of the battery,
  - the potential difference across the bulb,
  - the battery's internal resistance.

## Extension problems

9. Prove the *maximum power theorem*, that the maximum power drawn from a battery of e.m.f.  $\varepsilon$  and internal resistance  $r$  occurs when the circuit resistance  $R = r$ . What fraction of the energy supplied by the chemical energy of the battery is transferred to the circuit in this case?



Except where otherwise noted, this work is licensed under  
<http://creativecommons.org/licenses/by-nc-sa/4.0/>